

# ECE 20100 – Spring 2018

## Exam #1

February 8, 2018

**Section (include on scantron)**

Michelusi (9:30) – 0001

Tan (1:30) – 0004

Li (10:30) – 0005

Hosseini (12:30) – 0006

Cui (11:30) – 0007

Kildishev (12:30) – 0008

Liu (8:30) – 0009

Zhu (3:30) – 0010

### **Instructions**


1. DO NOT START UNTIL TOLD TO DO SO.
2. Write your name, section, professor, and student ID# on your **Scantron** sheet. We may check PUIDs.
3. This is a CLOSED BOOKS and CLOSED NOTES exam.
4. The use of a TI-30X IIS calculator is allowed.
5. If extra paper is needed, use the back of test pages.
6. Cheating will not be tolerated. Cheating in this exam will result in, at the minimum, an F grade for the course. In particular, **continuing to write after the exam time is up is regarded as cheating.**
7. If you cannot solve a question, be sure to look at the other ones, and come back to it if time permits.
8. ***All of the problems*** on Exam #1 provide evidence for satisfaction of this ECE 20100 Learning Objective:
  - i) An ability to analyze linear resistive circuits.

The minimum score needed to satisfy this objective will be posted on Blackboard after the exam has been graded. Remediation options will be posted in Blackboard if you fail to satisfy any of the course outcomes.

**By signing the scantron sheet, you affirm you have not received or provided assistance on this exam.**
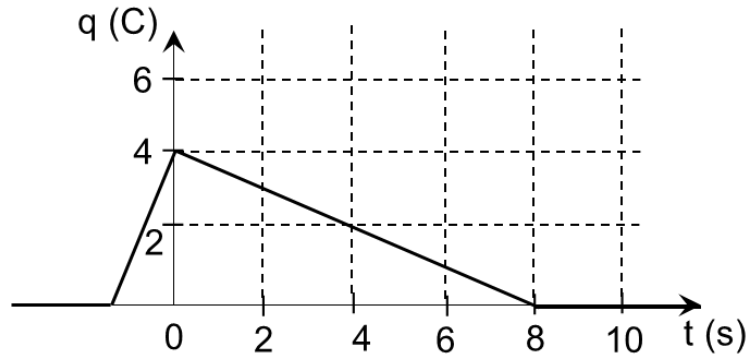
### Question 1


Charge flowing through a wire as a function of time is shown in the figure. Find the current flowing through the wire between 2 and 4 seconds (in A).



- (1) -5
- (2) -2
- (3) -1
- (4) -0.5
- (5) 0.5
- (6) 1
- (7) 2
- (8) 5
- (9) None of the above
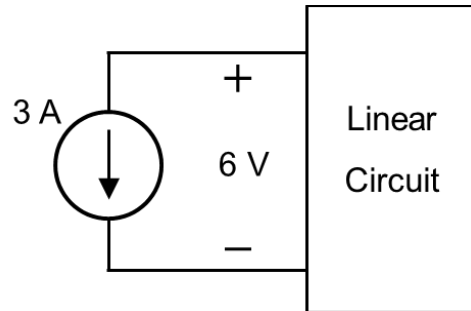
### Question 2

In the circuit shown below, find the power *delivered* by the current source (in W).



(1) -18

(2) -12

(3) -6

(4) -3

(5) 3

(6) 6


(7) 12

(8) 18

(9) None of the above
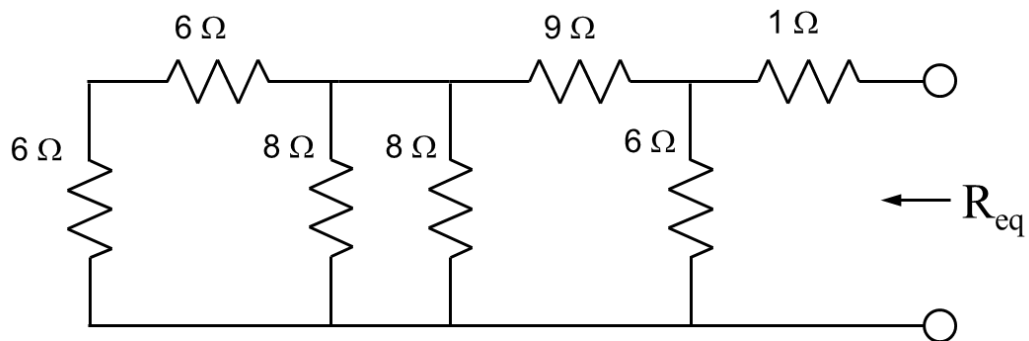
### Question 3


Find the equivalent resistance for the circuit shown (in Ohm).



- (1) 1
- (2) 2
- (3) 3
- (4) 4
- (5) 5**
- (6) 6
- (7) 7
- (8) 8
- (9) None of the above
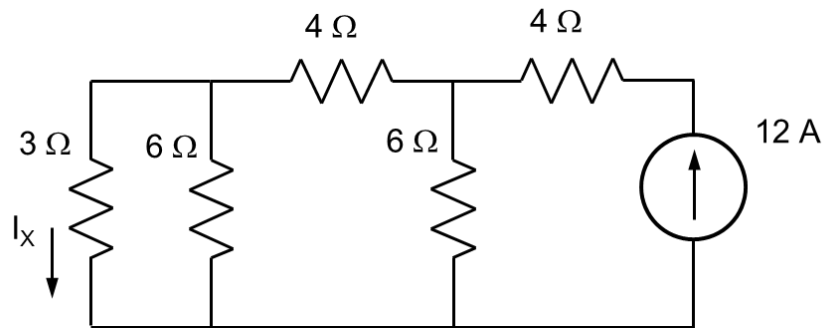
#### Question 4


Find the current  $I_X$  (in A) in the circuit shown.



- (1) 1
- (2) 2
- (3) 3
- (4) 4
- (5) 6
- (6) 8
- (7) 9
- (8) 12
- (9) None of the above
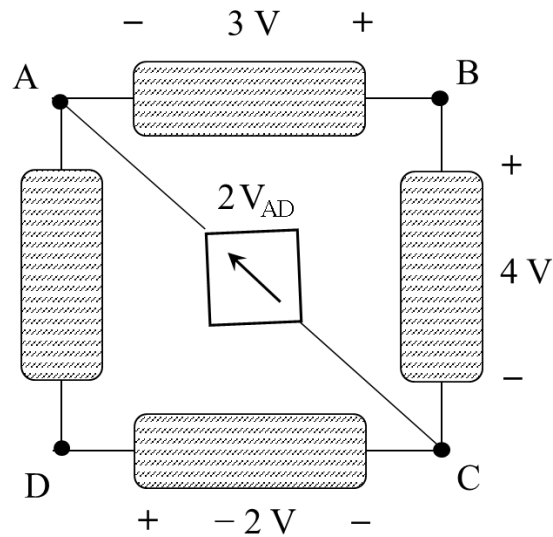
### Question 5


The shaded boxes below are generalized circuit elements (resistors or sources). Find the power *delivered* by the dependent current source (in W).



- (1) -2
- (2) -4
- (3) -6
- (4) 2
- (5) 4
- (6) 6
- (7) 8
- (8) 0
- (9) None of the above
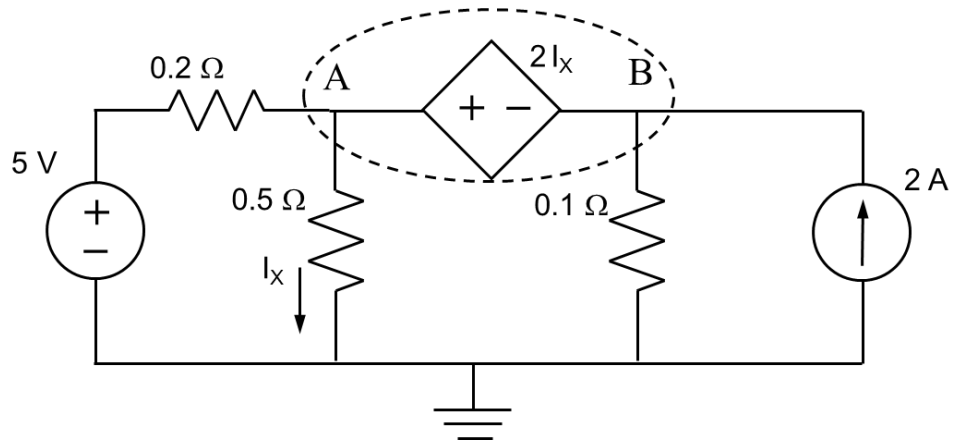
### Question 6


In the circuit shown, a supernode is drawn around nodes A and B (dashed line). Find the correct nodal equation for the supernode.



- (1)  $0.1 V_A + 10 V_B = 23$
- (2)  $0.2 V_A + 0.1 V_B = 27$
- (3)  $3 V_A + 10 V_B = 27$
- (4)  $3 V_A + 0.1 V_B = 23$
- (5)  $5 V_A + 10 V_B = 23$
- (6)  $0.5 V_A + 0.1 V_B = 27$
- (7)  $7 V_A + 10 V_B = 27$
- (8)  $7 V_A + 0.1 V_B = 23$
- (9) None of the above
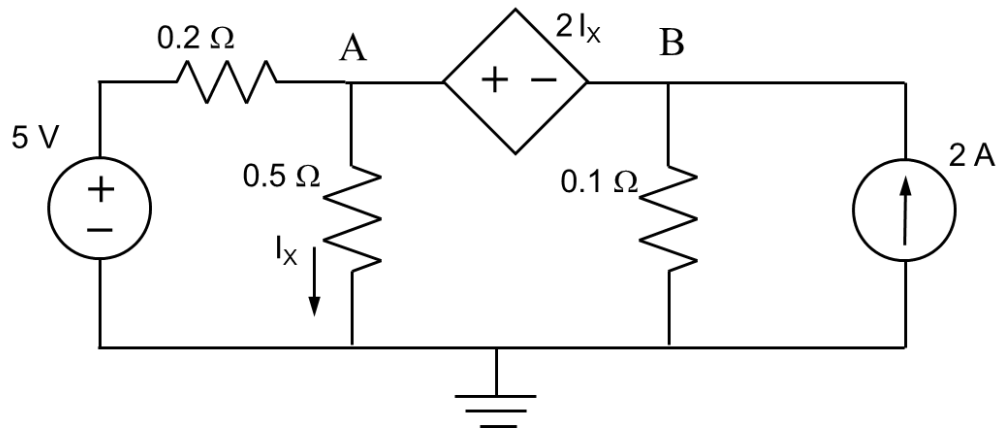
### Question 7

Find the equation that best represents the relationship between node voltages  $V_A$  and  $V_B$  (in V).




- (1)  $V_A + V_B = 0$
- (2)  $2 V_A + V_B = 0$
- (3)  $3 V_A + V_B = 0$
- (4)  $4 V_A + V_B = 0$
- (5)  $5 V_A + V_B = 0$
- (6)  $V_A + V_B = V_A$
- (7)  $2 V_A - V_B = 0$
- (8)  $5 V_A - V_B = 0$
- (9) None of the above


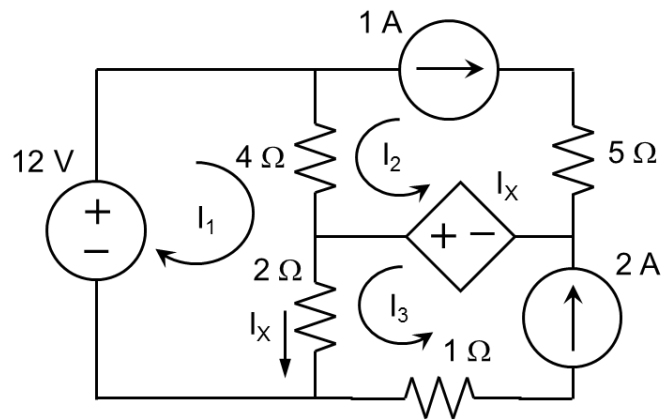
### Question 8

In the circuit shown below, find the loop current  $I_1$  (in A).




- (1) 1
- (2) 2
- (3) 3
- (4) 4
- (5) 5
- (6) 6
- (7) 7
- (8) 8
- (9) None of the above

### Question 9

Initial values for the voltage ( $V_1$ ) and current ( $I_2$ ) sources in the circuit shown produce an output potential,  $V_O$ , equal to 16 V.  $V_O$  is a linear function of  $V_1$  and  $I_2$  according to the equation,

$$V_O = A V_1 + B I_2$$

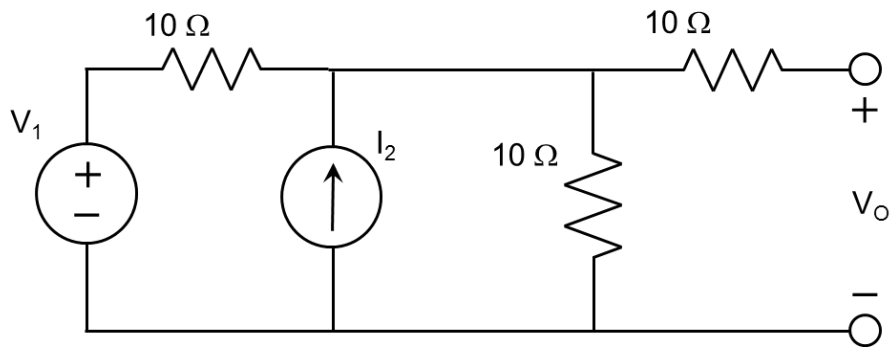
If doubling  $I_2$  changes  $V_O$  to 20 V when  $V_1$  remains constant, find  $V_1$  (in V).



- (1) 6
- (2) 8
- (3) 12
- (4) 16
- (5) 18
- (6) 20
- (7) 21
- (8) 24**
- (9) None of the above
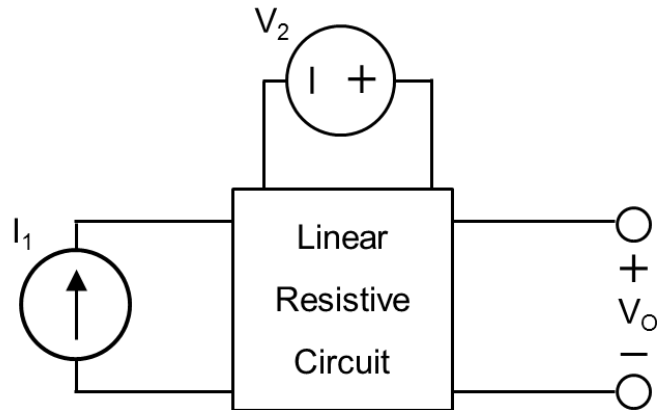
### Question 10

The linear resistive circuit below contains only resistors and dependent sources. Measurements of  $V_O$  for different input excitations are tabulated below. Find  $V_O$  when  $I_1 = 0.2 \text{ A}$  and  $V_2 = -2 \text{ V}$  (in V).




$I_1$	$V_2$	$V_O$
0.1 A	0	8 V
0	4 V	2 V

- (1) 6
- (2) 8
- (3) 12
- (4) 14
- (5) 15
- (6) 16
- (7) 17
- (8) 18
- (9) None of the above
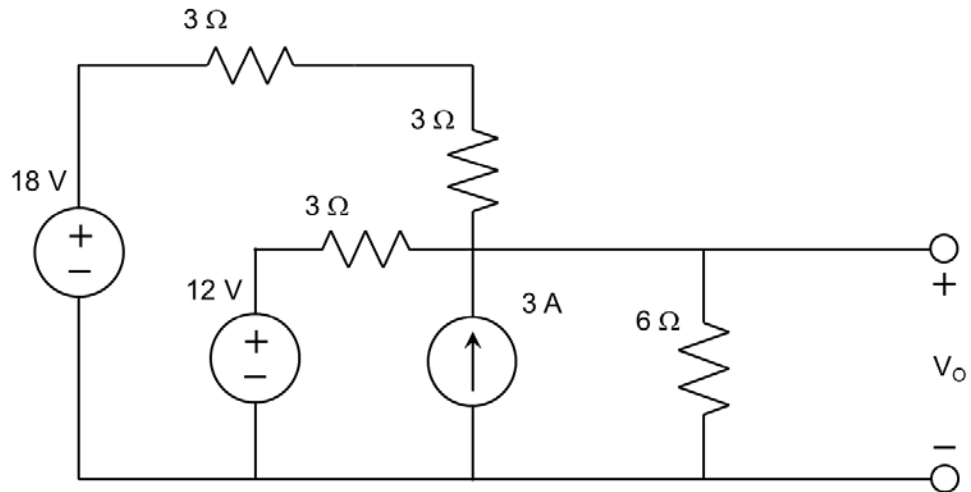
### Question 11


In the circuit below, find  $V_O$  (in V). [Hint: source transformations may be useful]




- (1) 6
- (2) 8
- (3) 9
- (4) 10
- (5) 12
- (6) 15**
- (7) 16
- (8) 18
- (9) None of the above
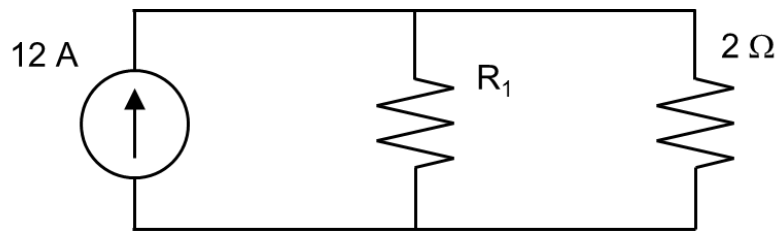
### Question 12

A resistor of unknown value,  $R_1$ , is connected to a  $2\ \Omega$  resistor and a  $12\text{ A}$  independent current source as shown below. In this configuration, the  $2\ \Omega$  resistor absorbs  $128\text{ W}$ .



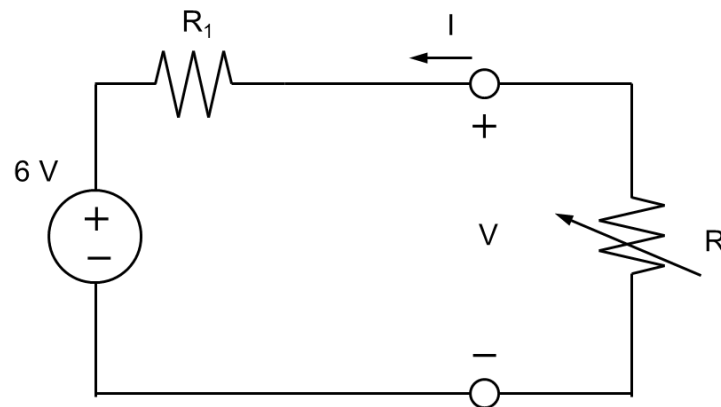The same resistor is subsequently connected to a variable resistor ( $R$ ) and voltage source as shown below. Find the correct current-voltage (I-V) relationship for this configuration.



- (1)  $I = 2\text{ V} + 1.5$
- (2)  $I = 0.33\text{ V} + 6$
- (3)  $I = 0.25\text{ V} + 1.5$
- (4)  $I = 3\text{ V} + 1.5$
- (5)  $I = 2\text{ V} - 6$
- (6)  $I = 0.33\text{ V} - 6$
- (7)  $I = 0.25\text{ V} - 1.5$
- (8)  $I = 3\text{ V} - 6$
- (9) None of the above